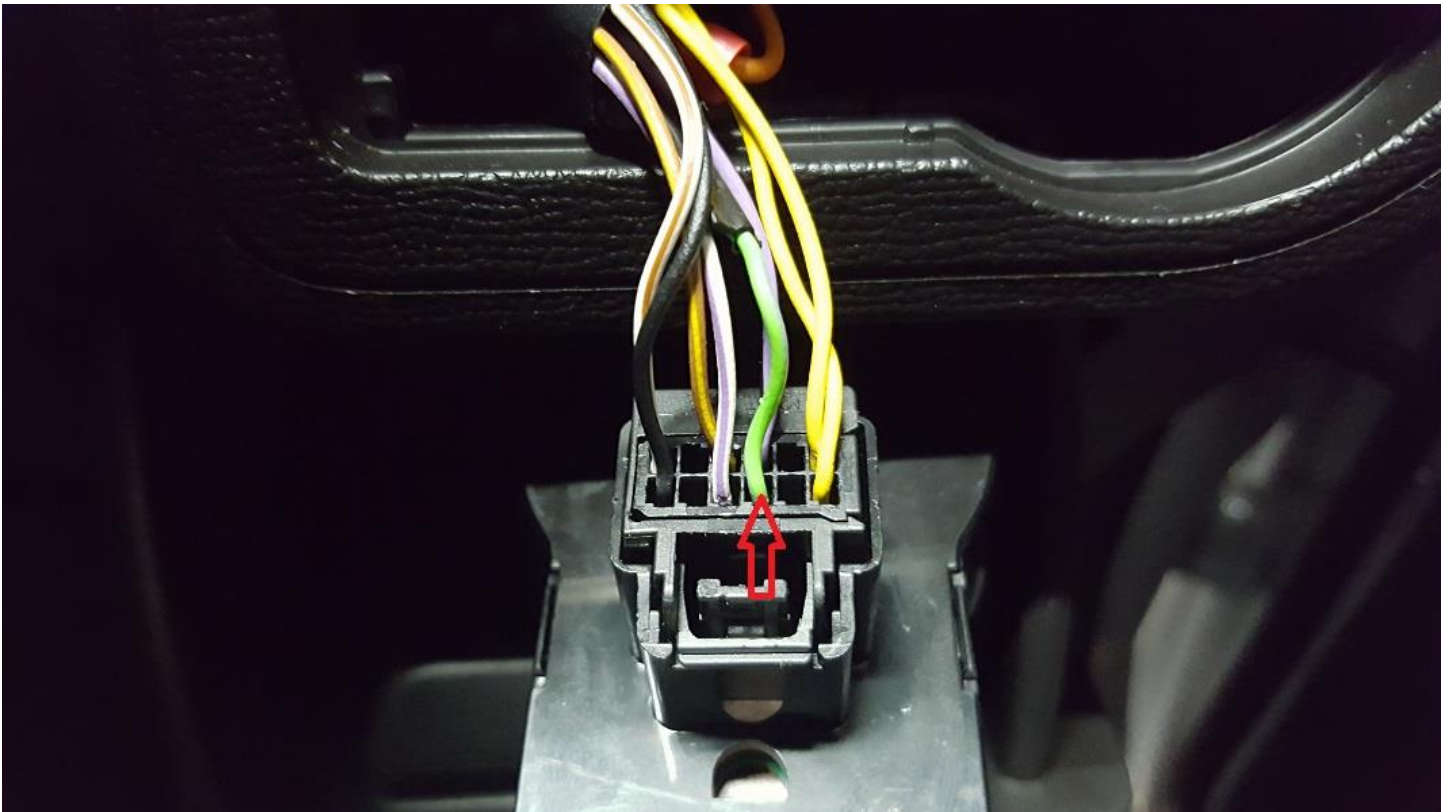


On the Colorado headlight switch you cut this green wire




And connect each side of the cut green wire to the auto headlight module shown here



I used crimp connectors on the green wires in the vehicle and ran longer wires to the module so I could package it all up in the plastic box.

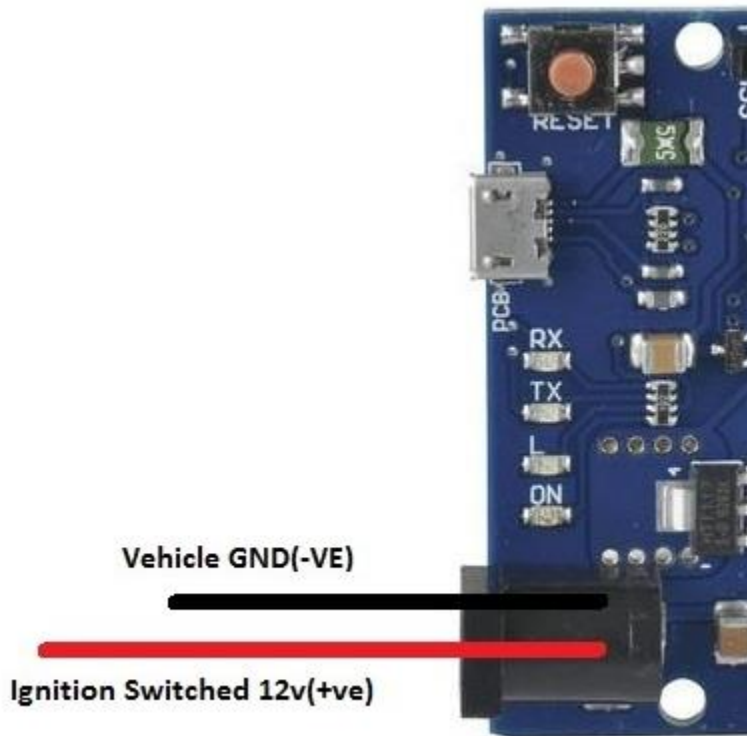The power for the module must be connected to an ignition switched power source so when the vehicle is off the module is not powered up, the positive wire is the middle pin of the plug.



If you don't have any old plugs that fit the power plug on the Arduino mainboard you might need to buy one that fits from jaycar, I used an old scrap one from a desktop hard drive.

